 


Computer Organization & Design Laboratory (20IC209P)

Project Report Submitted to

Pandit Deendayal Energy University, Gandhinagar

for



Bachelor of Technology

in

Information and Communication Technology
Department

Submitted by

DHANDHUKIYA HARSH (22BIT144)

Course Faculty

Dr. Gangaprasad Pandey

Dr. Ankur Changela

Dr. Manoj Yadav

PANDIT DEENDAYAL ENERGY UNIVERSITY, GANDHINAGAR – 382007,
India

- **AIM: -**
To design Central Processing Unit – CPU to perform various logical and arithmetic operations.

- **APPARATUS: -**
Logisim Software

- **SPECIFICATIONS: -**
 - There are certain registers like TR, AC, DR and IR that is used in this circuit design is 16-bit registers.
 - PC and AR both are 12-bit register itself.
 - Memory which is used in this CPU is 4Kx16 (there is 12-bits of address lines using 12-bit registers).

- **THEORY: -**
 - In broadly summarize, this entire circuit could be divided into three different parts or units which is known as **Arithmetic Logic Unit (ALU)** based on its individual operations; Arithmetic Unit, Logical Unit and Shift Operations.
 - The Arithmetic unit simply performs a basic mathematical operation in the CPU such as Addition, Subtraction, Add with carry, sub with carry, transfer, Increment and Decrement.
 - The Logical units executes all of the logical operations occurs in the CPU like AND, OR, XOR & NOT as well.
 - Last unit is Shift operations which simply performs the arithmetic shift. Logical shift and circular shift tasks in the CPU.
 - In order to design this CPU, we used as well as refer several Register Transfer Language (RTL) instructions which is as per the following;

TABLE 5-6 Control Functions and Microoperations for the Basic Computer

Fetch	$R'T_0$: $AR \leftarrow PC$
	$R'T_1$: $IR \leftarrow M[AR], PC \leftarrow PC + 1$
Decode	$R'T_2$: $D_0, \dots, D_7 \leftarrow \text{Decode } IR(12-14),$ $AR \leftarrow IR(0-11), I \leftarrow IR(15)$
Indirect	D_7IT_3 : $AR \leftarrow M[AR]$
Interrupt:	
	$T_0T_1T_2(IEN)(FGI + FGO)$: $R \leftarrow 1$
	RT_0 : $AR \leftarrow 0, TR \leftarrow PC$
	RT_1 : $M[AR] \leftarrow TR, PC \leftarrow 0$
	RT_2 : $PC \leftarrow PC + 1, IEN \leftarrow 0, R \leftarrow 0, SC \leftarrow 0$
Memory-reference:	
AND	D_0T_4 : $DR \leftarrow M[AR]$ D_0T_5 : $AC \leftarrow AC \wedge DR, SC \leftarrow 0$
ADD	D_1T_4 : $DR \leftarrow M[AR]$ D_1T_5 : $AC \leftarrow AC + DR, E \leftarrow C_{out}, SC \leftarrow 0$
LDA	D_2T_4 : $DR \leftarrow M[AR]$ D_2T_5 : $AC \leftarrow DR, SC \leftarrow 0$
STA	D_3T_4 : $M[AR] \leftarrow AC, SC \leftarrow 0$
BUN	D_4T_4 : $PC \leftarrow AR, SC \leftarrow 0$
BSA	D_5T_4 : $M[AR] \leftarrow PC, AR \leftarrow AR + 1$ D_5T_5 : $PC \leftarrow AR, SC \leftarrow 0$
ISZ	D_6T_4 : $DR \leftarrow M[AR]$ D_6T_5 : $DR \leftarrow DR + 1$ D_6T_6 : $M[AR] \leftarrow DR, \text{ if } (DR = 0) \text{ then } (PC \leftarrow PC + 1), SC \leftarrow 0$
Register-reference:	
	$D_7I'T_3 = r$ (common to all register-reference instructions)
	$IR(i) = B_i$ ($i = 0, 1, 2, \dots, 11$)
	r : $SC \leftarrow 0$
CLA	rB_{11} : $AC \leftarrow 0$
CLE	rB_{10} : $E \leftarrow 0$
CMA	rB_9 : $AC \leftarrow \overline{AC}$
CME	rB_8 : $E \leftarrow \overline{E}$
CIR	rB_7 : $AC \leftarrow \text{shr } AC, AC(15) \leftarrow E, E \leftarrow AC(0)$
CIL	rB_6 : $AC \leftarrow \text{shl } AC, AC(0) \leftarrow E, E \leftarrow AC(15)$
INC	rB_5 : $AC \leftarrow AC + 1$
SPA	rB_4 : If $(AC(15) = 0)$ then $(PC \leftarrow PC + 1)$
SNA	rB_3 : If $(AC(15) = 1)$ then $(PC \leftarrow PC + 1)$
SZA	rB_2 : If $(AC = 0)$ then $PC \leftarrow PC + 1$
SZE	rB_1 : If $(E = 0)$ then $(PC \leftarrow PC + 1)$
HLT	rB_0 : $S \leftarrow 0$
Input-output:	
	$D_7IT_3 = p$ (common to all input-output instructions)
	$IR(i) = B_i$ ($i = 6, 7, 8, 9, 10, 11$)
	p : $SC \leftarrow 0$
INP	pB_{11} : $AC(0-7) \leftarrow INPR, FGI \leftarrow 0$
OUT	pB_{10} : $OUTR \leftarrow AC(0-7), FGO \leftarrow 0$
SKI	pB_9 : If $(FGI = 1)$ then $(PC \leftarrow PC + 1)$
SKO	pB_8 : If $(FGO = 1)$ then $(PC \leftarrow PC + 1)$
ION	pB_7 : $IEN \leftarrow 1$
IOF	pB_6 : $IEN \leftarrow 0$

- o It is outlining the different parts of the CPU and the instructions it can carry out. Here is a breakdown of the table along with how it relates to your CPU design:

TABLE 5-2 Basic Computer Instructions

Symbol	Hexadecimal code		Description
	<i>I</i> = 0	<i>I</i> = 1	
AND	0xxx	8xxx	AND memory word to <i>AC</i>
ADD	1xxx	9xxx	Add memory word to <i>AC</i>
LDA	2xxx	Axxx	Load memory word to <i>AC</i>
STA	3xxx	Bxxx	Store content of <i>AC</i> in memory
BUN	4xxx	Cxxx	Branch unconditionally
BSA	5xxx	Dxxx	Branch and save return address
ISZ	6xxx	Exxx	Increment and skip if zero
CLA	7800		Clear <i>AC</i>
CLE	7400		Clear <i>E</i>
CMA	7200		Complement <i>AC</i>
CME	7100		Complement <i>E</i>
CIR	7080		Circulate right <i>AC</i> and <i>E</i>
CIL	7040		Circulate left <i>AC</i> and <i>E</i>
INC	7020		Increment <i>AC</i>
SPA	7010		Skip next instruction if <i>AC</i> positive
SNA	7008		Skip next instruction if <i>AC</i> negative
SZA	7004		Skip next instruction if <i>AC</i> zero
SZE	7002		Skip next instruction if <i>E</i> is 0
HLT	7001		Halt computer
INP	F800		Input character to <i>AC</i>
OUT	F400		Output character from <i>AC</i>
SKI	F200		Skip on input flag
SKO	F100		Skip on output flag
ION	F080		Interrupt on
IOF	F040		Interrupt off

o Control Unit:

- ❑ The control unit is responsible for fetching, decoding, and executing instructions.
- ❑ Based on the opcode (operation code) in the instruction register (IR), the control unit generates various control signals to other parts of the CPU.
- ❑ In the image, the table shows the micro-operations for each instruction which are the basic building blocks for the control unit.

o Data Path:

- ❑ The data path is the circuitry that performs the ALU operations and data transfers directed by the control unit.
- ❑ The data path includes the arithmetic logic unit (ALU), registers, and memory
- ❑ The ALU performs arithmetic and logical operations on data.
- ❑ Registers store data for temporary use.
- ❑ Memory stores data and instructions.

o Instruction set architecture (ISA):

- ❑ This refers to the set of instructions that your CPU can understand and execute. The table shows a limited ISA with instructions for Load (LDA), Store (STA), Add (ADD), and Branch (BUN) operations.

o Instruction Fetch:

- ❑ The CPU retrieves instructions from the computer's memory using the Instruction Pointer (IP) or Program Counter (PC).

o Instruction Decode:

- ❑ It decodes the fetched instruction to determine the operation and operands involved.

o Operand Fetch:

- ❑ If needed, the CPU retrieves operands from memory or registers.

o Execution:

- ❑ It performs the operation based on the decoded instruction and fetched operands.

o Write Back:

- ❑ If necessary, the CPU stores the result of the operation.


o Repeat:

- The CPU repeats these steps for the next instruction, following the program's flow.

- o Throughout these steps, the CPU interacts with other components like memory, registers, and input/output devices. Components like the ALU, Control Unit, and Register File help manage data and instructions.

The CPU operates based on instructions stored in memory, executing them sequentially until the program is completed or terminated.

■ **CIRCUIT DIAGRAM: -**

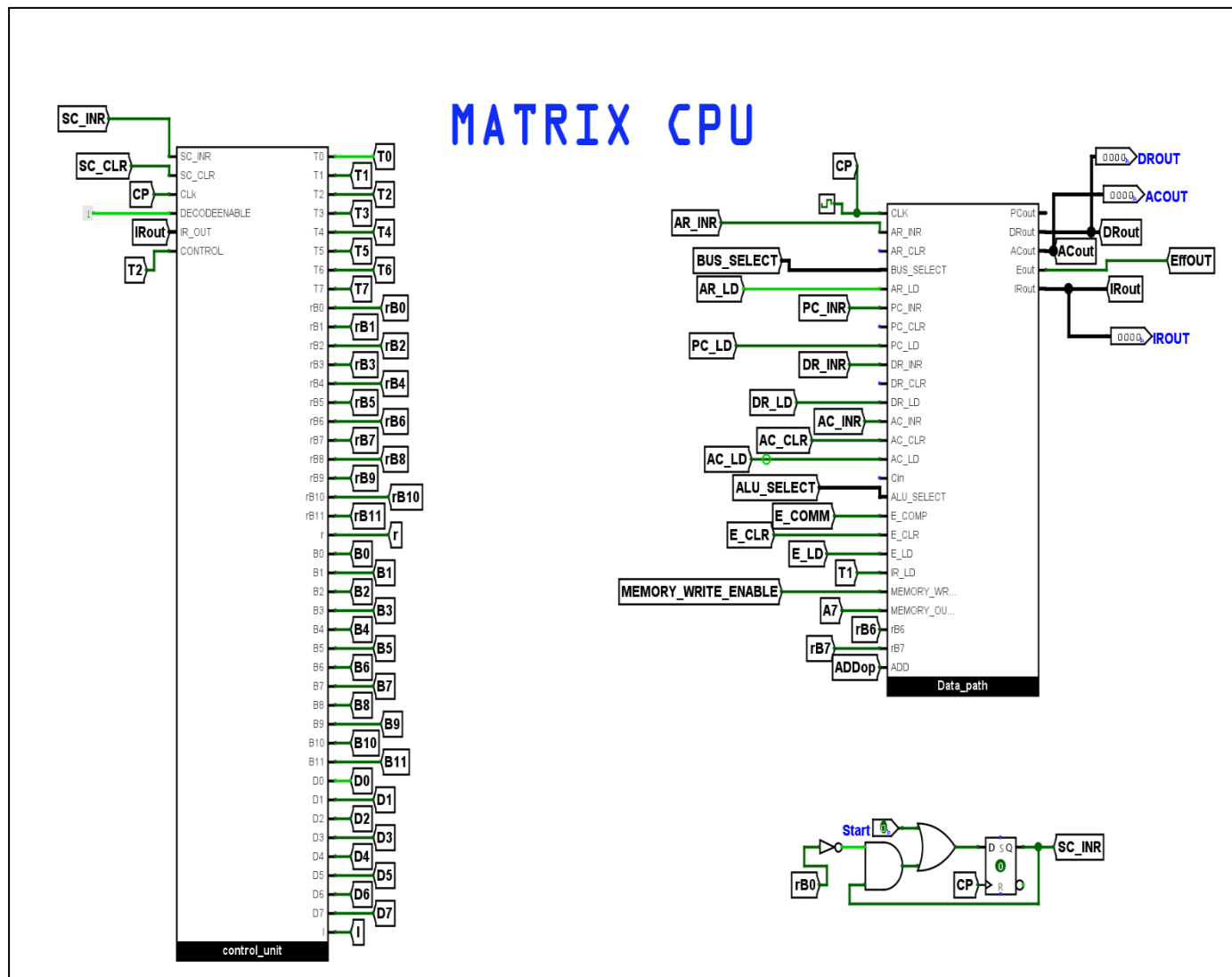



■ CIRCUIT DESCRIPTION: -

 1. 12-bit & 16-bit Register

A 12-bit register is a digital circuit component capable of storing and manipulating 12 binary bits, each representing 0 or 1. It is typically made up of 12 flip-flops or memory cells organized sequentially, allowing for separate read and write operations at the bit level. It can store up to 12 bits of data and represent decimal values from 0 to 4095. 12-bit registers are widely used in digital systems for data storing, buffering, and arithmetic operations. They are ideal for moderate precision needs.


A 16-bit register stores and manipulates 16 binary values, each representing a 0 or 1. It usually consists of 16 flip-flops or memory cells arranged sequentially stores and retrieves 16 bits of data. This register is useful in digital systems for storing data, buffering, and doing arithmetic. It can store 16 bits of data and represent decimal numbers from 0 to 65535. 16-bit registers are commonly used in computer systems and microprocessors for managing data and instructions, with a reasonable precision requirement.



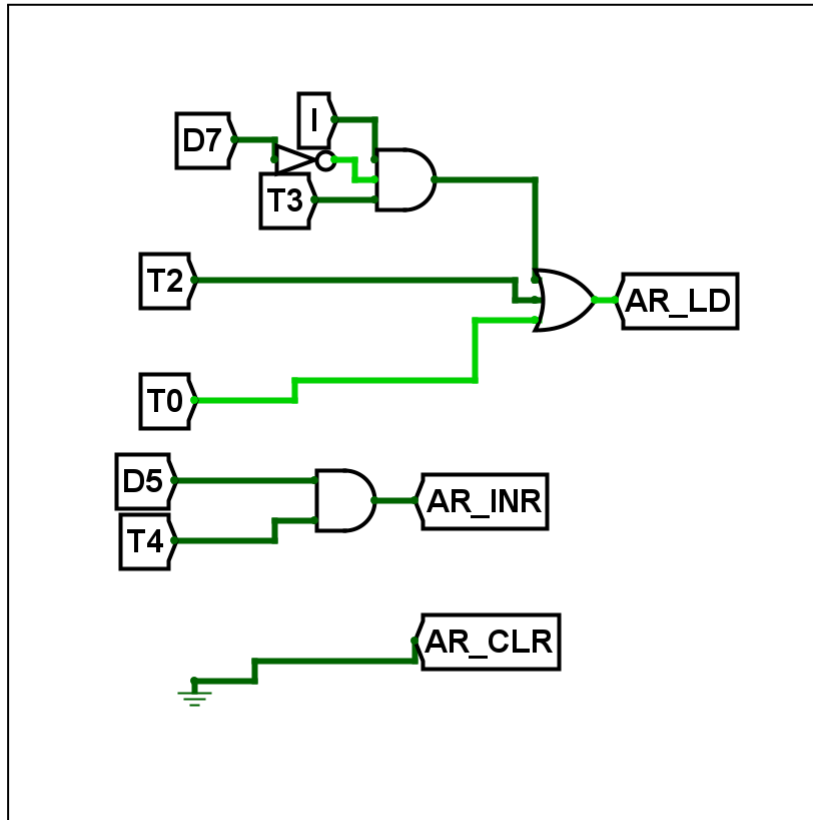

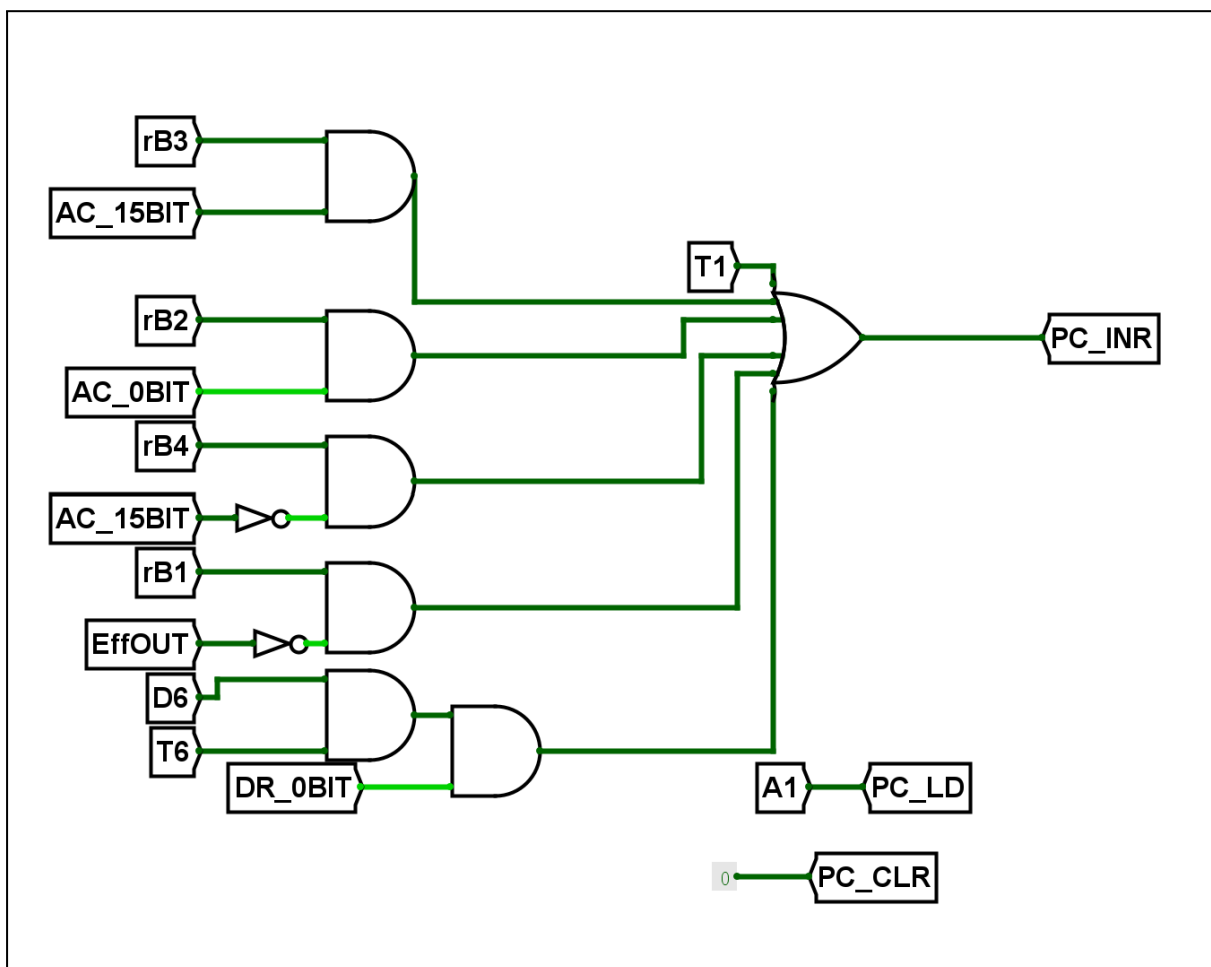3. PC

The program counter, also known as the instruction pointer, can also be referred to as the instruction address register, instruction counter, or simply the instruction itself. A sequencer is a processor register that indicates a computer's current program sequence. This contains the address of the following instruction. This is a 12-bit register that stores the address of the next instruction.




4. DR

A data register is a digital circuit component used in computers to store data. A register stores CPU-processed data.


Microprocessors utilize data registers. Data can be temporarily stored on other computing systems while it is being read from memory, calculated, or altered. Binary values can represent data, including numbers, characters, and other information.

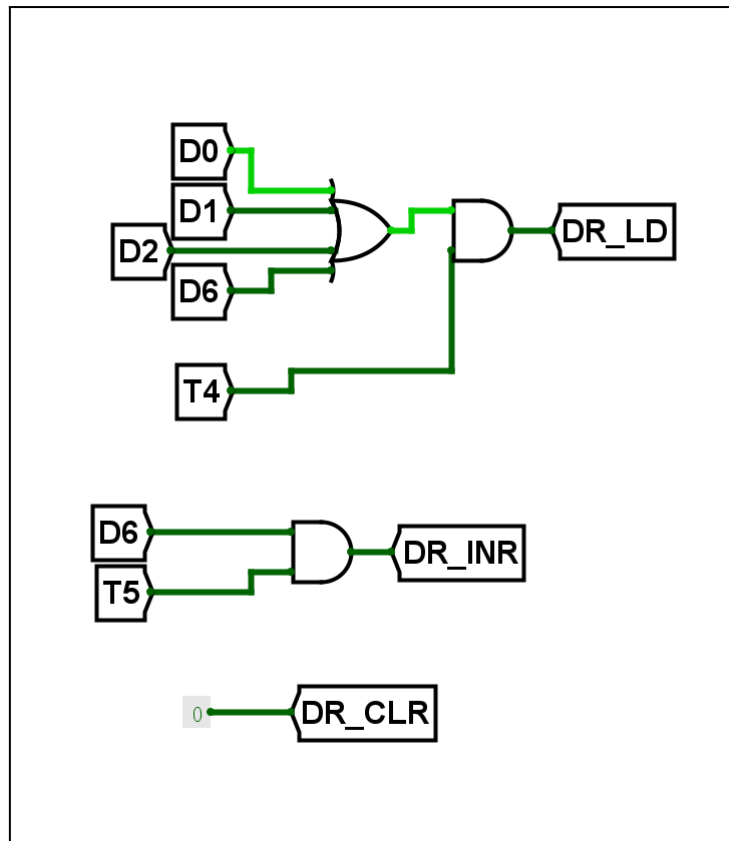Data registers store data temporarily during instruction execution and are essential for CPU data processing. Data contained in a register can be manipulated and transferred to other registers or memory locations.



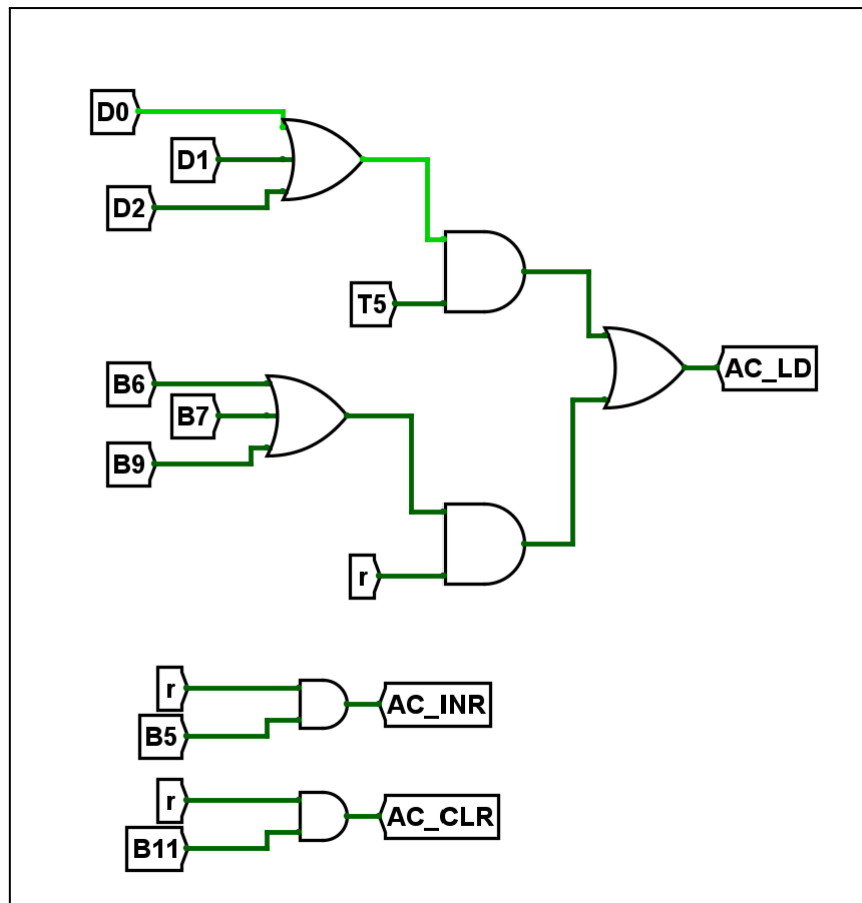5. AC

An accumulator is a CPU register that performs arithmetic and logic operations. This is a temporary storage area for intermediate results or operands used during instruction execution. The accumulator serves as a working register for arithmetic and logic operations. Data is received from memory or input/output devices, processed by the CPU, and then saved in the accumulator or transferred to other registers or memory locations.



6. IR

This register stores all instructions for decoding and connects to the control and timing unit to decode the four MSBs. This is a 16-bit register, as this CPU's data size is 16 bits. The most significant bit (MSB) is 'I' (Mode bit), followed by three instruction bits (14-12) and twelve address bits (11-0). The instruction register stores the opcode (operation code) and other information, such as operands or addressing modes.




7. TR

Only temporary registers can be read and written many times within a single instruction. Temporary registers support single-write and triple-read access. Instructions can have up to three temporary registers as input source operands. This register stores temporary data, such as the next program instruction, between interrupt cycles. However, this register is not used in this project due to the absence of interrupts. This register is 16-bit in capacity, matching the CPU's data size.

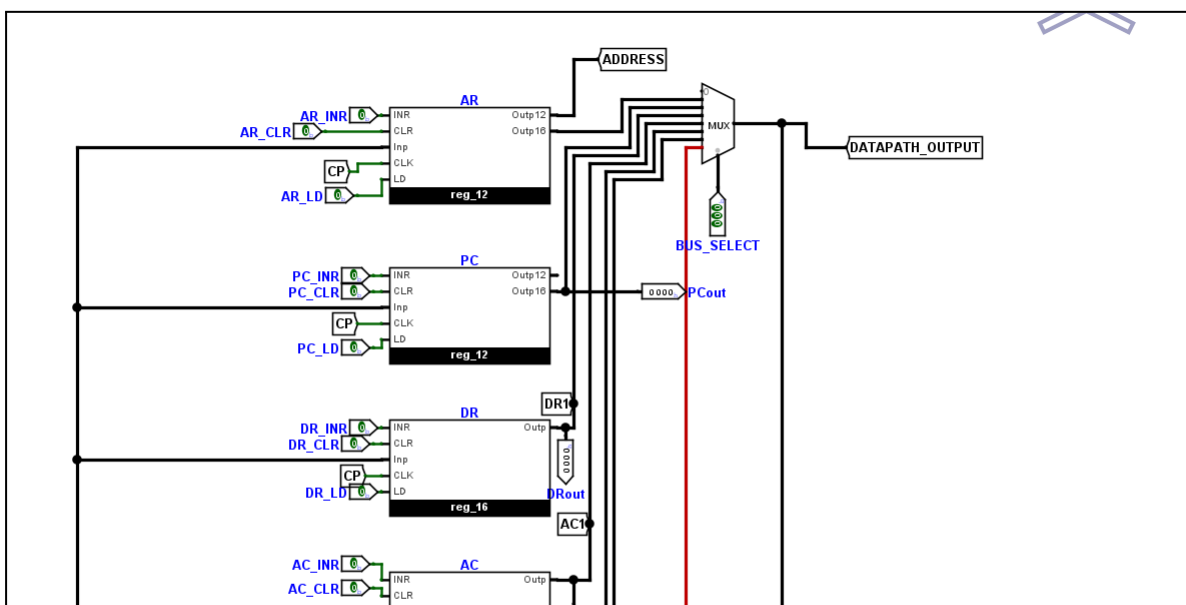
8. Common Bus



The 16-bit common bus is governed by selection inputs S2, S1, and S0. Each bus input is associated with a decimal number, indicating the binary configuration required for the corresponding register selection. These binary configurations, represented by Boolean variables x1 through x7, activate specific gate structures to choose the register or memory for the bus. For instance, when x1 equals 1, the binary sequence S2S1S0 must be 001, resulting in the selection of the output of AR for the bus. This setup facilitates efficient memory transfer between registers and memory within the CPU. Compared to using separate lines for each register's input and output, the common bus reduces complexity and cost. A decoder is employed to determine which register's data will be present on the common bus.



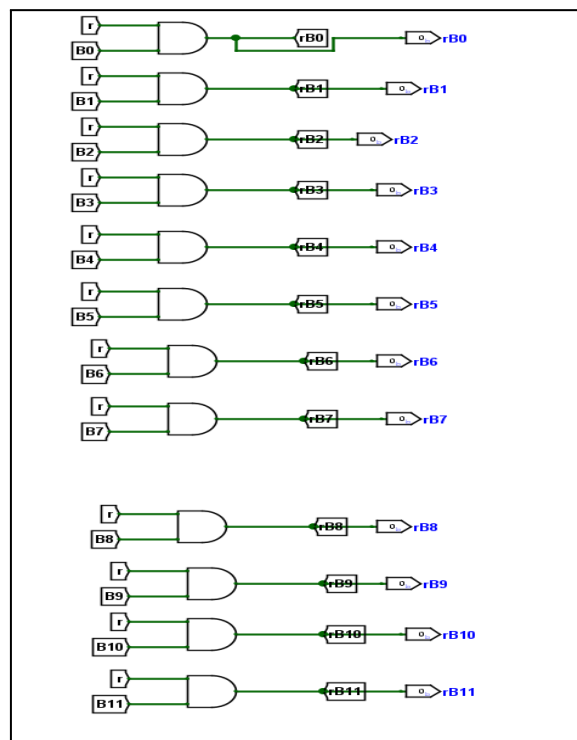9. Timing and Control Unit

The Timing and Control Unit decodes IR data and generates control signals. This includes a 4-bit sequence counter and a decoder that creates timing signals. The 'I' in the MSB of IR indicates the mode. Bits 14 to 12 determine the instruction, which is then sent into a decoder to form a control signal. In memory reference instructions, bits 11 through 0 are address bits, but in register reference instructions, they are control signals. The generated signals are used in the hardwired control unit, which includes control logic for various registers.



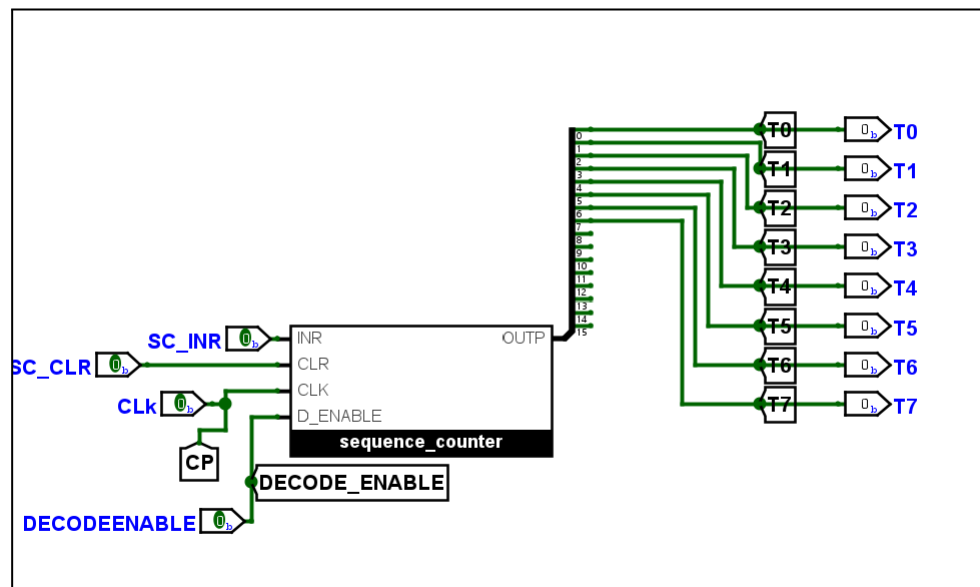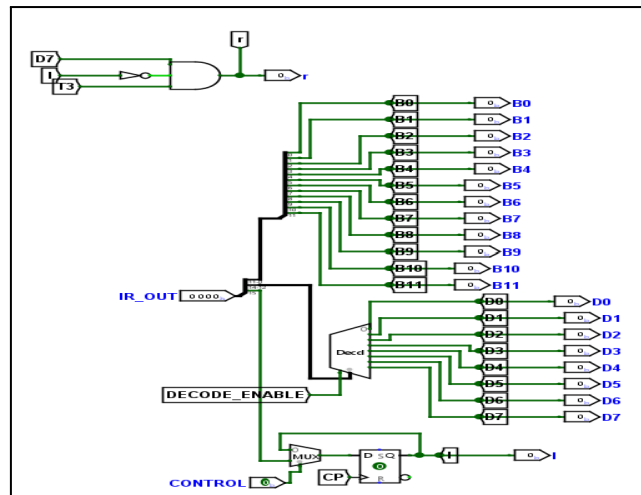

■ **CONCLUSION: -**

This project explains fundamental aspects essential for discerning hardware digital processing units, encompassing the replacement of microoperations by computer registers. Additionally, it elucidates the functionality of pivotal components such as the Arithmetic Logic Unit (ALU), registers, and multiplexers. Consequently, it can be asserted that the design of the 16-bit CPU exhibits success, having effectively addressed and integrated these foundational elements.